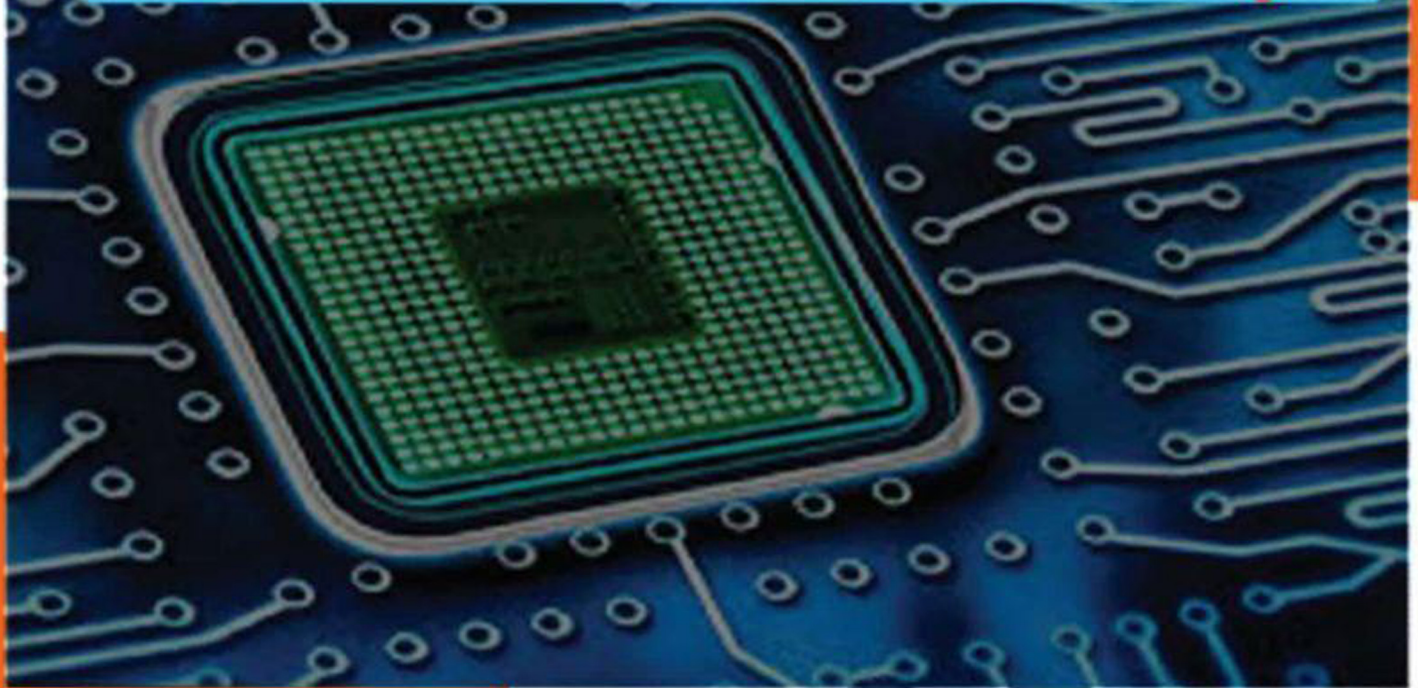


# Electrical Engineering - Optional For IAS (UPSC)



**Digital Electronics - 2015-2021**


**INDAINCIVILS**  
**Online IAS Academy**



**INDIANCIVILS.COM - 90000 18804**

## UPSC – ELECTRICAL Engineering optional – 2015 Questions

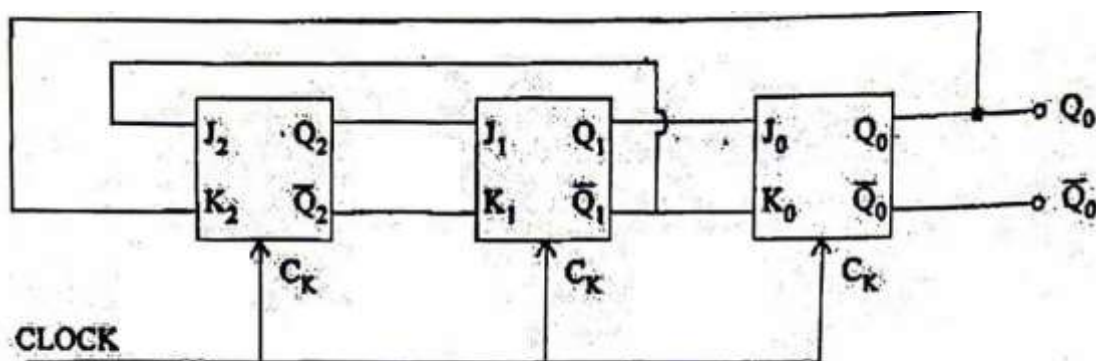1. Obtain all the possible minimal functions for:  $F = \sum(0, 2, 3, 4, 5, 7)$ . [10M]
2. Divide by N counter is shown in the figure below. If Initially  $Q_0 = 0, Q_1 = 1, Q_2 = 0$ , what is the value of N? [20M]



Figure

## UPSC – ELECTRICAL Engineering optional – 2016 Questions

1. Minimize the SOP terms given for a Boolean function  $f(A, B, C, D) = \sum m(2, 3, 8, 10, 11, 12, 14, 15)$

Implement the minimized function using NAND gates alone. [10M]

2. What is a PLA? Realize the following functions using an appropriate PLA: [10M]

$$\begin{aligned} f_1 &= AB + CD \\ f_2 &= \bar{A}B + A\bar{B} \\ f_3 &= AD + BC + \bar{B}D \end{aligned}$$

## UPSC – ELECTRICAL Engineering optional – 2017 Questions

1. For the Boolean function  $F(W, X, Y, Z) = \sum(0, 2, 5, 6, 7, 8, 10, 13)$  [20M]
  - (i) find all the prime implicants;
  - (ii) give minimal representation;
  - (iii) find minimal two-level realization using NAND gates only.

2. Prove that  $\bar{A}B + \bar{B}C + \bar{A}C = \bar{A}B + \bar{B}C$ . [10M]

3. Find the state transition diagram and realization using J-K flip-flops to count Mod 7 in the following sequence: 000, 001, 011, 100, 101, 111 [20M]

### UPSC – ELECTRICAL Engineering optional – 2018 Questions

1. Convert the following logic equation to NAND logic and draw the circuit using NAND gates:  $Z = (\bar{A} + \bar{B}) + C + A(\bar{B} + \bar{C})$  [20M]

2. Convert a D flip flop to function as an S-R flip flop .Draw the circuit. [10M]

3. Design a synchronous counter using D flip flop that counts in the following sequence:

6, 3, 5, 0, 2, 6, 3, 5, 0, 2, 6, ...

Draw the circuit. [20M]

### UPSC – ELECTRICAL Engineering optional – 2019 Questions

1. Simplify the following expression using Boolean algebra: [10M]

$$Y = AC + A(B + C) + C(B + C)$$

and draw the logic diagram for reduced expression.

2. Implement Astable Multi vibrator using NAND gates and explain its operation. [10M]

3. Reduce the combinational logic circuit shown in Figure 7(d) to a minimum form. [10M]

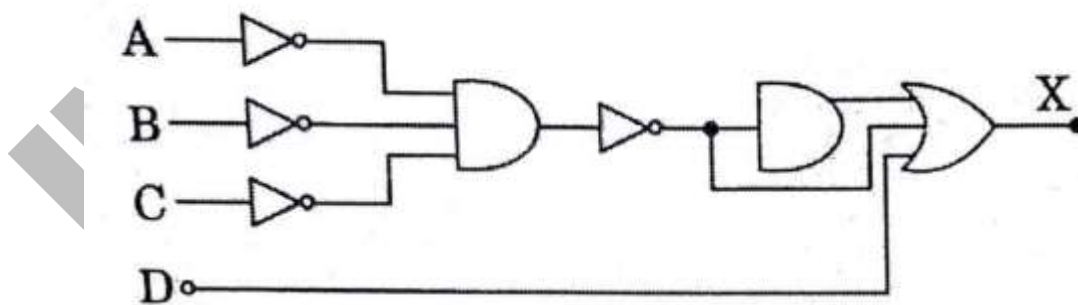


Figure 3.

4. Draw the block diagram of a single slope type A/D converter and explain its principle of operation. [20M]



## UPSC – ELECTRICAL Engineering optional – 2020 Questions

1. Implement the following Boolean functions with a  $4 \times 3$  Programmable Logic Array (PLA): [10M]

$$F_1 = \bar{B}\bar{C} + A\bar{B}$$

$$F_2 = AB\bar{C} + A\bar{B}C\bar{D}$$

$$F_3 = \bar{A}\bar{B}\bar{C}D + A\bar{B}CD$$

2. Design a combinational circuit to implement the minimal sum-of-products of the logic function  $F = \sum_{WXYZ}(1, 2, 3, 4, 5, 7, 11, 13)$ . [10M]
3. Design a synchronous sequential circuit with D-flip-flops for a state diagram shown in Figure 4(b). [20M]

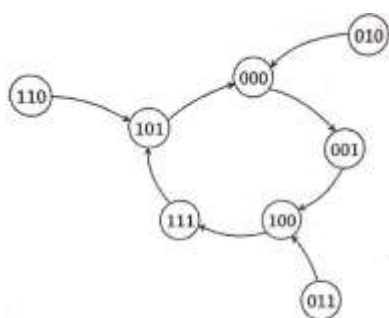


Figure 4(b)

## UPSC – ELECTRICAL Engineering optional – 2021 Questions

1. Consider the four variables logic function defined as follows:  
 $F(A, B, C, D) = \bar{A}C + \bar{A}D + \bar{B}C + \bar{B}D + AB\bar{C}\bar{D}$   
 Assuming input variables as A, B, C and D, propose a logic circuit using only three logic gates to implement the function. [10M]
2. Consider the circuit shown in Figure 2(c) below. Let inputs A, B and C be all initially LOW. Output Y is supposed to go HIGH only when A, B and C go HIGH in a certain sequence. Determine the sequence that will make Y go HIGH. Modify this circuit to use D-Flip-flops. [10M]

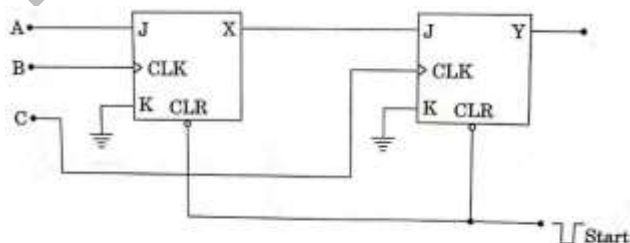


Figure 2(c)

3. (i) Verify by determining the logic equation for the output and by constructing the truth table for the logic circuit shown in Figure 4(b).

- (ii) Use an 8 to 1 multiplexer and logic gates to implement the following function: [20M]

$$F(A, B, C, D, E) = \sum m(0, 1, 2, 4, 5, 6, 7, 13, 14, 20, 21, \dots, 28, 29, 30, 31)$$

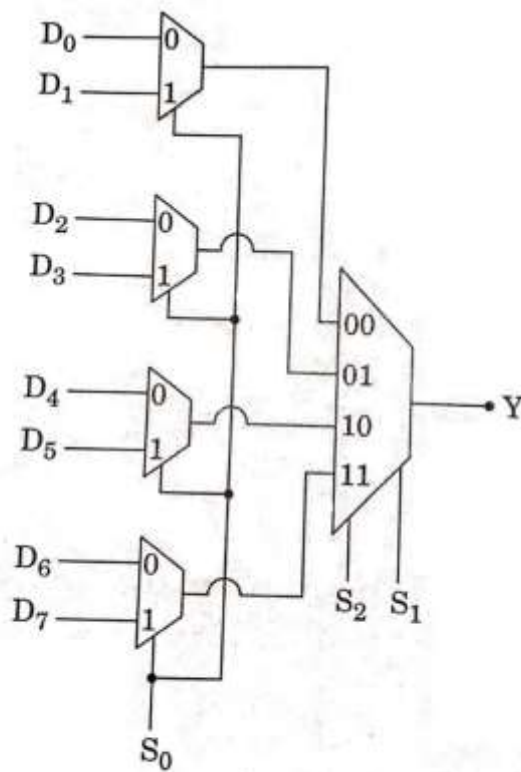


Figure 4(b)

**INDIANCIVILS.COM**

**An online IAS Academy**

**ONLINE LIVE COURSES WE OFFER:**

- 1.MATHEMATICS - OPTIONAL**
- 2.TELUGU LITERATURE -OPTIONAL**
- 3. PHYSICS OPTIONAL**
- 4. ELECTRICAL OPTIONAL**

**Subscribe to our youtube channel: INDIANCIVILS.COM**

**E-mail : [info@indiancivils.com](mailto:info@indiancivils.com)**

**Phone : +91-9000018804 / 9000018827**

**Facebook : <https://www.facebook.com/indiancivilsdotcom>**